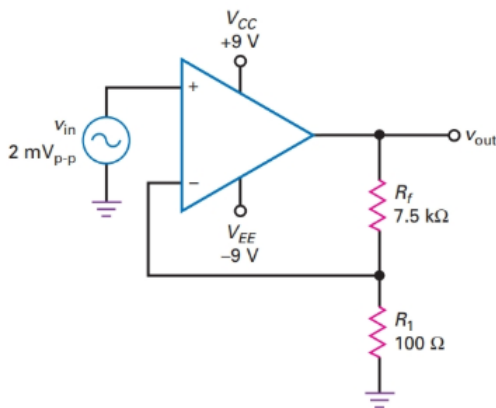


# Negative feedback

Jiwook Kim

**1** In Fig. 17-16, the op amp has an  $R_{in}$  of  $3\text{ M}\Omega$  and an  $R_{CM}$  of  $500\text{ M}\Omega$ . What is the closed-loop input impedance? Use an  $A_{VOL}$  of  $200,000$  for the op amp.




The open loop input resistance  $R_{in} = 3\text{ M}\Omega$   
 The common mode input resistance  $R_{CM} = 500\text{ M}\Omega$   
 The open loop voltage gain =  $A_{vol} = 200,000$

$$B = V_2 / V_{out} = R_1 / (R_1 + R_f) = 100\Omega / (100\Omega + 7.5\text{ k}\Omega) = 0.013$$

The feedback factor is  $0.013$

$$Z_{in} = (1 + A_{vol}B) * R_{in} || R_{CM} = [(1 + (200000)(0.013)) (3\text{ M}\Omega)] || 500\text{ M}\Omega = 470\text{ M}\Omega.$$

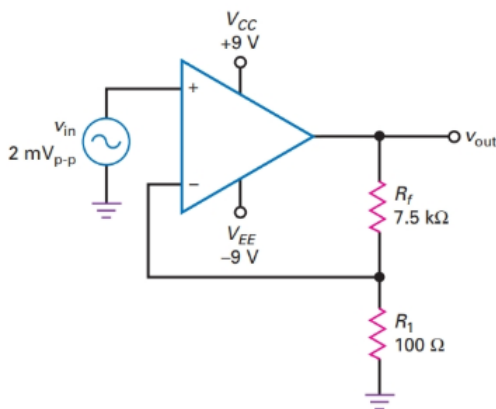**2** What is the closed-loop output impedance in Fig. 17-16? Use an  $A_{VOL}$  of  $75,000$  and an  $R_{out}$  of  $50\text{ V}$ .



The open loop output resistance  $R_{out} = 50\Omega$

The open loop voltage gain =  $A_{vol} = 75,000$

$$B = V_2 / V_{out} = R_1 / (R_1 + R_f) = 100\Omega / (100\Omega + 7.5\text{ k}\Omega) = 0.013$$

The feedback factor is  $0.013$

$$Z_{out} = R_{out} / (1 + A_{vol} * B) = 50\Omega / (1 + (75000) 0.13) = 0.051\Omega$$

**3** A VCVS amplifier uses an LM324 with  $(1 + A_{VOL} * B) = 1000$  and  $f_{2(OL)} = 2\text{ Hz}$ . What is the closed-loop bandwidth?

$$f_{2OL} = 2\text{ hz}$$

$$(1 + A_{vol} * B) = 1000$$

The closed loop bandwidth of VCVS amplifier is

$$f_{2CL} = f_{2OL} * (1 + A_{vol} * B) = (2\text{ hz}) (1000) = 2\text{ kHz}$$

**4** An ICVS amplifier uses an LM318 with  $A_{VOL} = 20,000$  and  $f_{2(OL)} = 750\text{ Hz}$ . What is the closed-loop bandwidth

It is given that  $f_{2OL} = 750\text{ Hz}$   
 Open loop voltage gain  $A_{VOL} = 20000$

The closed loop bandwidth of ICVS(current controlled voltage source) amplifier is

$$f_{2CL} = f_{2OL} * (1 + A_{vol}) = (1 + 20000) 750\text{ Hz} = 15\text{ MHz}$$

**5** An ICIS amplifier uses a TL072 with  $f_{2(OL)} = 120\text{ Hz}$ . If  $(1 + A_{VOL}B) = 5000$ , what is the closed-loop bandwidth?


$$f_{2OL} = 120\text{ hz}$$

$$(1 + A_{vol} * B) = 5000$$

The closed loop bandwidth of ICIS(current controlled current source) amplifier is

$$f_{2CL} = f_{2OL} * (1 + A_{vol} * B) = (120\text{ Hz}) (5000) = 600\text{ kHz}$$

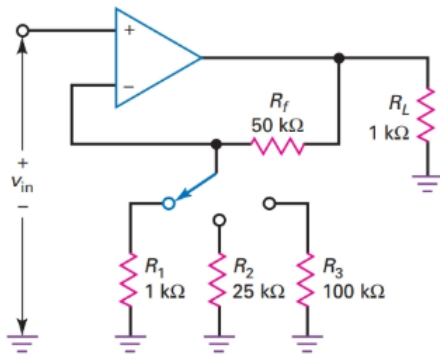6 In Fig. 17-22, what is the output voltage for each position of the switch if the input voltage is 10 mV?



Non inverting amplifier

$$A = 1 + R_f/R$$

$$A_1 = 1 + 50\text{k}\Omega/1\text{k}\Omega = 51$$

$$V_{out1} = V_{in} * A_1 = 10\text{mV} * 51 = 510\text{mV}$$

$$A_2 = 1 + 50\text{k}\Omega/25\text{k}\Omega = 3$$

$$V_{out2} = V_{in} * A_2 = 10\text{mV} * 3 = 30\text{mV}$$

$$A_3 = 1 + 50\text{k}\Omega/100\text{k}\Omega = 1.5$$

$$V_{out3} = V_{in} * A_3 = 10\text{mV} * 1.5 = 15\text{mV}$$