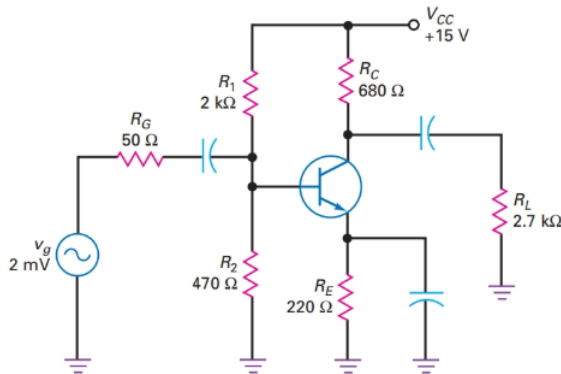


Power Amplifier

Jiwook Kim

1 What is the DC collector resistance in Fig. 10-38? What is the DC saturation current?




Collector resistance.

$$R_C = 680\Omega$$

DC saturation current.

$$I_{Cmax} = V_{CC}/(R_E + R_C) = 15V/(680\Omega + 220\Omega) = 16.67mA$$

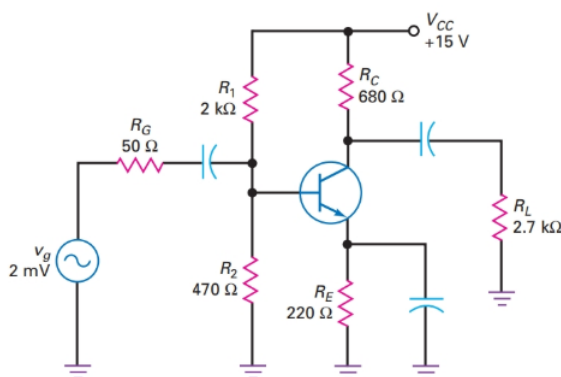2 In Fig. 10-38, what is the AC collector resistance? What is the AC saturation current?



AC collector resistance

$$R_C || R_L = 680\Omega || 2.7k\Omega = 540\Omega$$

AC saturation current

$$V_{BB} = V_{CC} * R_2 / (R_1 + R_2) = 15V * 470/(2000+470) = 2.85V$$

$$V_E = V_{BB} - 0.7V = 2.15V$$


$$I_{CQ} \approx I_E$$

$$I_E = V_E/R_E = 9.77mA$$

$$V_{CE} = V_{CC} - I_{CQ} * R_C - V_E = 15V - 9.77mA * 680\Omega - 2.15V = 6.2V$$

$$I_{C(sat)} = I_{CQ} + V_{CE}/r_c = 9.77mA + 6.2V/0.54k\Omega = 21.25mA$$

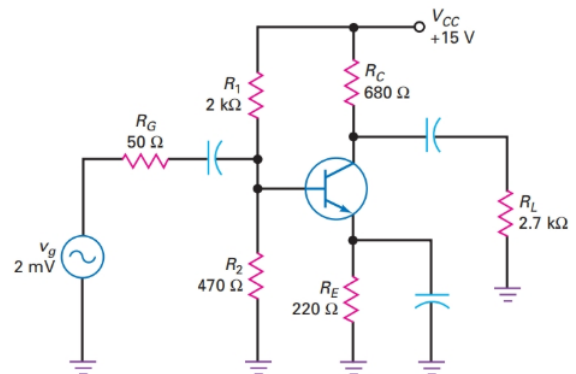3 What is the maximum peak-to-peak output in Fig. 10-38?



$$V_{BB} = V_{CC} * R_2 / (R_1 + R_2) = 15V * 470/(2000+470) = 2.85V$$

$$V_E = V_{BB} - 0.7V = 2.15V$$

$$I_{CQ} \approx I_E$$

$$I_E = V_E/R_E = 9.77mA$$

$$V_{CE} = V_{CC} - I_{CQ} * R_C - V_E = 15V - 9.77mA * 680\Omega - 2.15V = 6.2V$$

$$I_{C(sat)} = I_{CQ} + V_{CEQ}/r_c = 9.77mA + 6.2V/0.54k\Omega = 21.25mA$$

MPP(maximum peak to peak output) < 15V

$$I_{CQ} * r_c = 9.77mA * 0.54k\Omega = 5.3V$$

$$V_{EQ} = 6.2V$$

$$MPP(maximum peak to peak output voltage) = 2 * 5.3V = 10.6V$$

4 An amplifier has an input power of 4mW and output power of 2 W. What is the power gain?

$$A_P = p_{out}/p_{in} = 2W / 4mW = 500$$


5 If an amplifier has a peak-to-peak output voltage of 15V across a load resistance of 1 k Ω , what is the power gain if the input power is 400 μ W?

$$P_{out} = V^2/(8R_L) \\ (15V)^2/(8*1k\Omega) = 28.125mW$$

$$A_P = P_{out}/P_{in} = 28.125mW/400\mu W = 70.3$$

The power gain of the amplifier is 70.3

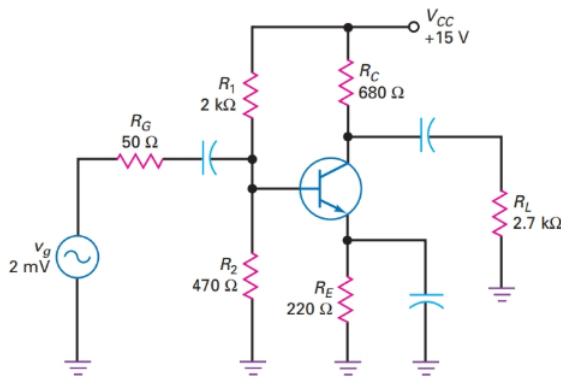6 What is the current drain in Fig. 10-38.



$$V_{BB} = 470\Omega/(2k\Omega + 470\Omega) * 15 = 2.85V$$

$$V_{EE} = 2.85V - 0.7V = 2.15V$$


$$I_{EE} = V_{EE}/R_{EE} = 2.15V/220\Omega = 9.77mA$$

$$I_{Bias} = V_{CC}/(R_1 + R_2) = 15V/2470\Omega = 6.07mA$$

The drain current is

$$I_{DC} = I_{Bias} + I_{CQ} = 6.07mA + 9.77mA = 15.84mA$$

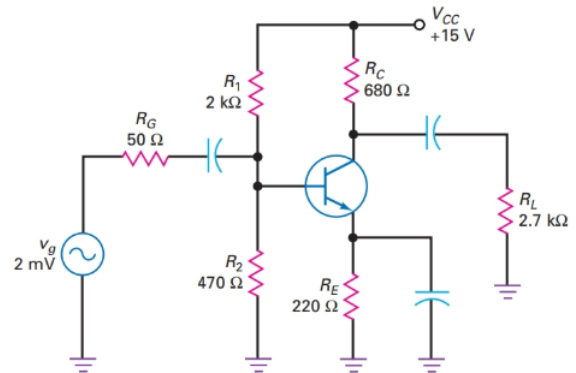7 What is the DC power supplied to the amplifier of Fig. 10-38?



$$V_B = R_2/(R_2 + R_1) 15V = 470/2470 * 15V = 2.85V$$

$$V_E = V_B - 0.7V = 2.15V$$

$$I_E = V_E/R_E = 2.15V/220\Omega = 9.77mA$$

$$I_{CQ} \approx I_E = 9.77mA$$


$$I_{bias} = V_{CC}/(R_1 + R_2)$$

$$I_{bias} = 15V/(2k\Omega + 470\Omega) = 6.07mA$$

$$I_{dc} = I_{bias} + I_{CQ} = 6.07mA + 9.77mA = 15.84mA$$

$$P_{DC} = V_{CC} * I_{DC} = 15V * 15.84mA = 237.6mW$$

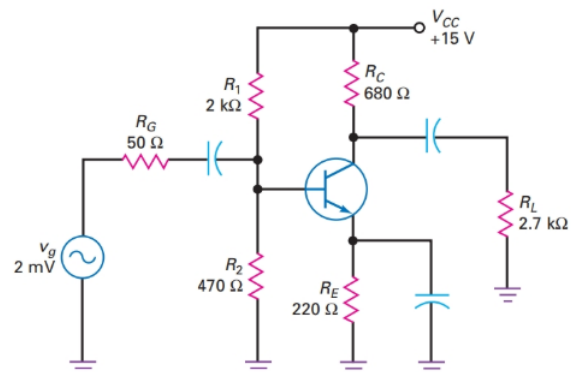8 The input signal of Fig. 10-38 is increased until maximum peak-to-peak output voltage is across the load resistor. What is the efficiency?



$$V_B = (470\Omega)/(2k\Omega + 470\Omega) * 15V = 2.85V$$

$$V_E = V_B - 0.7V = 2.85V - 0.7V = 2.15V$$

$$I_E = V_E/R_E = 2.15V/220\Omega = 9.77mA$$

$$= 15V - 9.77mA * 680\Omega = 8.36V$$

$$V_C = V_{CC} - I_{CQ} * R_C$$

$$= 15V - 9.77mA * 680\Omega = 8.36V$$

$$V_{CEQ} = V_C - V_E = 8.36V - 2.15V = 6.21V$$

$$r_c = R_C || R_L = 680\Omega || 2.7k\Omega = 543\Omega$$

MPP(maximum peak to peak output voltage) < 15V

$$MP(\text{maximum peak output voltage}) = I_{CQ} * R_C = 9.77mA * 543\Omega = 5.3V$$

or

$$V_{CEQ} = 6.21V$$

$$MPP = 2 * (MP) = 2 * 5.3V = 10.6V$$

$$I_{bias} = V_{cc} / (R_1 + R_2) = 15V / (2k\Omega + 470\Omega) = 6.07mA$$

$$I_{DC} = I_{bias} + I_{CQ} = 6.07mA + 9.77mA = 15.84mA$$

$$P_{DC} = V_{cc} * I_{dc} = 15V * 15.84mA = 237.6mW$$

$$P_{out(Max)} = (MPP)^2 / 8R_L = (10.6V)^2 / 8(2.7k\Omega) = 0.520 mW$$

$$\mu = P_{out} / P_{in} = 0.520 mW / 237.6mW = 0.022 = 2.2\%$$

9 What is the quiescent power dissipation in Fig. 10-3

$$V_B = 470\Omega / 2470\Omega * 15V = 2.85V$$

$$V_E = V_B - 0.7V = 2.15V$$

$$I_E = V_E / R_E = 9.77mA$$

$$I_{CQ} \approx I_E = 9.77mA$$

$$V_C = V_{CC} - I_{CQ} * R_C = 15V - 6.64V = 8.36V$$


$$V_{CEQ} = V_C - V_E = 8.36V - 2.15V = 6.21V$$

$$P_{DC} = V_{CEQ} * I_{CQ} = 6.21V * 9.77mA = 60.67mW$$

Quiescent power dissipation is 60.67mW

10 If $V_{BE} = 0.7 V$ in Fig. 10-40, what is the dc emitter current

Figure 10-40

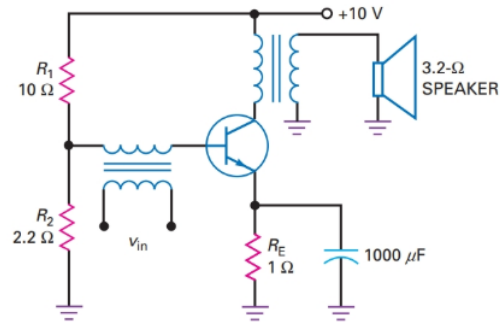

$$V_B = 2.2\Omega / 12.2\Omega * 15V = 1.8V$$

$$V_E = V_B - 0.7V = 1.1V$$


$$I_E = V_E / R_E = 1.1A$$

$$I_{CQ} \approx I_E = 1.1A$$

dc emitter current 1.1A

11 What is the quiescent collector current in Fig. 10-42?

Figure 10-42

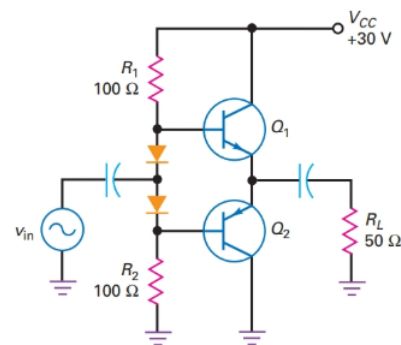

$$I_{bias} = (V_{CC} - 2 * V_{BE}) / (2R) = (30V - 2 * 0.7V) / (200\Omega) = 143 mA$$

quiescent collector current = 143mA

12 In Fig. 10-42, what is the maximum efficiency of the amplifier?

$$I_{bias} = (V_{CC} - 2 * V_{BE}) / (2R) = (30V - 2 * 0.7V) / (200\Omega) = 143 mA$$

quiescent collector current = 143mA

$$I_{c(sat)} = V_{CEQ} / R_L = (30V / 2) / 50\Omega = 0.3A$$

$$I_{c(average)} = I_{c(sat)} / \pi = 95.5mA$$

The total current drain

$$I_{dc} = I_{bias} + I_{average} = 143 \text{ mA} + 95.5 \text{ mA} = 238.5 \text{ mA}$$

$$P_{dc} = (V_{CC}) * (I_{DC}) = 30 \text{ V} * 238.5 \text{ mA} = 7.155 \text{ W}$$


The maximum ac output power is

$$P_{outmax} = (MPP)^2 / (8 * R_L) = 30^2 / (8 * 50 \Omega) = 2.25 \text{ W}$$

The efficiency of the amplifier

$$\mu = P_{outmax} / P_{in} * 100\% = 2.25 \text{ W} / 7.155 \text{ W} * 100\% = 31.5\%$$

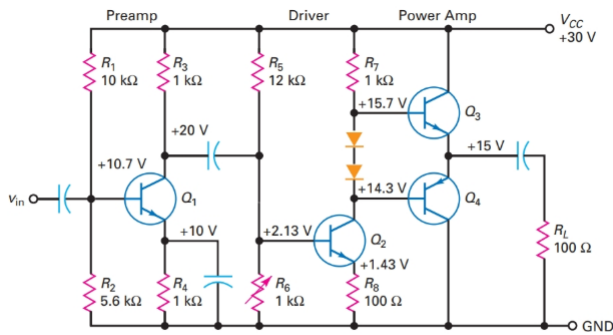13 What is the overall voltage gain for the three-stage amplifier in Fig. 10-43?



$$V_B = 10.7 \text{ V}$$

$$\text{Thus, } V_E = 10 \text{ V}$$

$$I_E = V_E / R_E = 10 \text{ V} / 1 \text{ k}\Omega = 10 \text{ mA}$$

$$r'_e = 25 \text{ mV} / I_E = 2.5 \Omega$$

$$V_{B2} = 2.13 \text{ V}$$

$$\text{Thus, } V_{E2} = 1.43 \text{ V}$$

$$I_{E2} = V_{E2} / R_E = 1.43 \text{ V} / 100 \Omega = 14.3 \text{ mA}$$

$$r'_{e(driver)} = 25 \text{ mV} / I_E = 1.75 \Omega$$

$$Z_{in2(base)} = \beta * r'_{e(driver)} = 200 * 1.75 = 350 \Omega$$

$$Z_{in(driver)} = Z_{in2(base)} || R_5 || R_6 = 350 \Omega || 12 \text{ k}\Omega || 1 \text{ k}\Omega = 254 \Omega$$

Voltage gain of the first stage

$$A_{v1} = (R_3 || Z_{in(driver)}) / r'_e = (1 \text{ k}\Omega || 250 \Omega) / 2.5 \Omega = 81$$

Voltage gain of a directly coupled amplifier and the voltage gain of second stage.


$$A_{v2} = R_7 / R_8 = 1 \text{ k}\Omega / 100 \Omega = 10$$

Third stage is push-pull amplifier stage, with a negative feedback. The voltage gain of push pull amplifier is 1.

$$A_v = A_{v1} * A_{v2} * A_{v3} = 81 * 10 * 1 = 810$$

The total voltage gain is 810

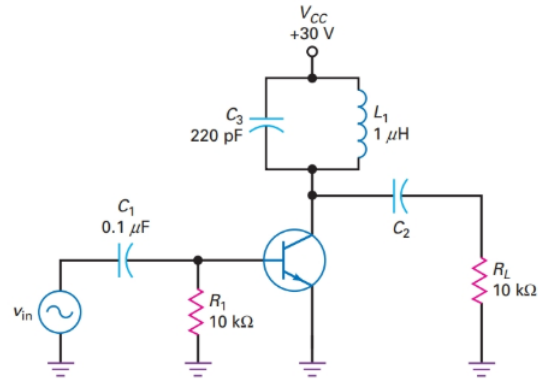14 What is the resonant frequency in Fig. 10-44.




Resonant frequency

$$L = 1 \mu \text{ H}$$

$$C = 220 \text{ pF}$$

$$f_r = 1 / (2\pi * (L * C)^{1/2}) = 1 / (2\pi * (1 \mu \text{ H} * 220 \text{ pF})^{1/2}) = 10.73 \text{ Mhz}$$

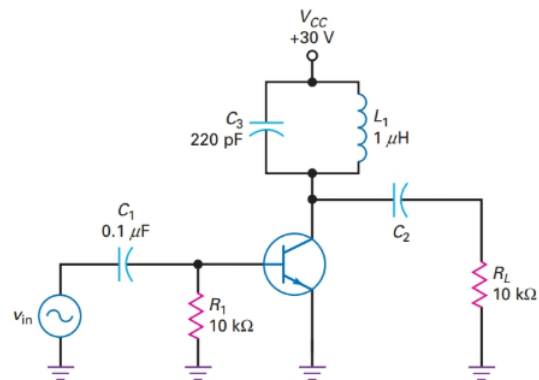15 What is the efficiency of Fig. 10-44 if the current drain is 0.4mA and the output voltage is 30V pp.



$$I_{DC} = 0.4 \text{ mA}$$

The output peak to peak voltage is 30V

$$P_{DC} = I_{DC} * V_{CC} = 30 \text{ V} * 0.4 \text{ mA} = 12 \text{ mW}$$

The ac output power

$$P_{out} = (MPP)^2 / (8 * R_L) = 30^2 / (8 * 10 \text{ k}\Omega) = 11.25 \text{ mW}$$

Efficiency

$$\mu = P_{out} / P_{in} * 100\% = 11.25 \text{ mW} / 12 \text{ mW} * 100\% = 93.75\%$$